

04. DIODES

- Physics of semiconductor
- p-n junction diode
- Diode rectifier circuits
- Other diode circuits

PHYSICS OF SEMICONDUCTOR


Semiconductor

- Resistivity: conductor: $\rho < 10^{-8} \Omega.m$
insulator: $\rho > 10^{11} \Omega.m$
- resistivity of semiconductors: $\rho = 10^{-6} \sim 10^4 \Omega.m$
- ρ varies over large range with temperature, voltage, impurity concentration, geometry, etc.

Intrinsic Semiconductor

- Si, Ge, GaAs, etc.
- Four valence electrons per atom
- Creation of electron-hole pairs by thermal excitation: $\propto e^{kT/E}$
- Conduction of free electrons and holes.


III	IV	V
⁵ B	⁶ C	⁷ N
¹³ Al	¹⁴ Si	¹⁵ P
³¹ Ga	³² Ge	³³ As
⁴⁹ In	⁵⁰ Sn	⁵¹ Sb
⁸¹ Tl	⁸² Pb	⁸³ Bi

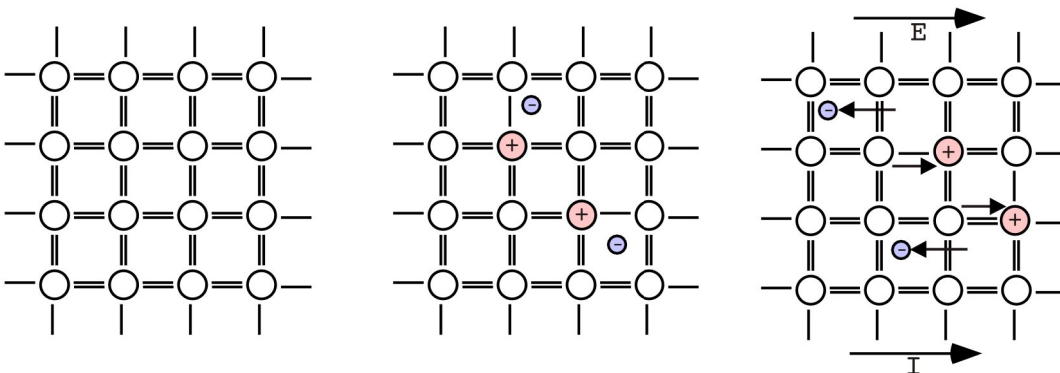


Extrinsic Semiconductor

- n-type semiconductor: doped by donor (e.g. group V elements) atoms.
- p-type semiconductor: doped by acceptor (e.g. group III elements) atoms.
- Donor atoms easily give up electrons, generating free electrons.
- Acceptor atoms easily take up electrons from neighbor, generating holes.

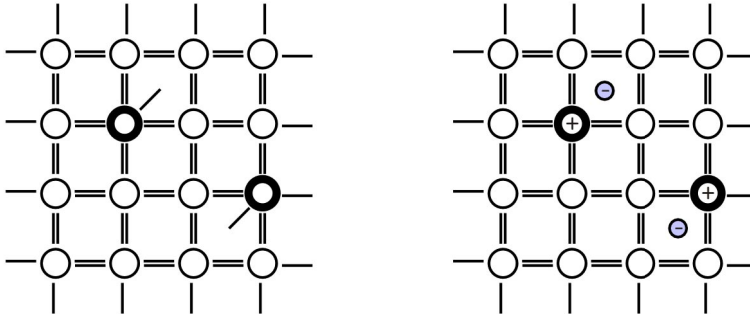n-type semiconductor w. donor atoms generate free electrons.



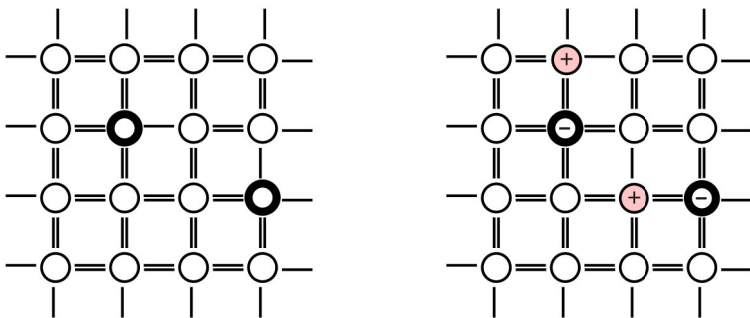
p-type semiconductor w. acceptor atoms generate holes.



p-n Junction Diode


- p-type and n-type semiconductors in contact
- Recombination of holes and electrons create depletion layer.
- Net charge density of depletion layer (dipolar layer) gives rise to electric field and potential gradient in the region.

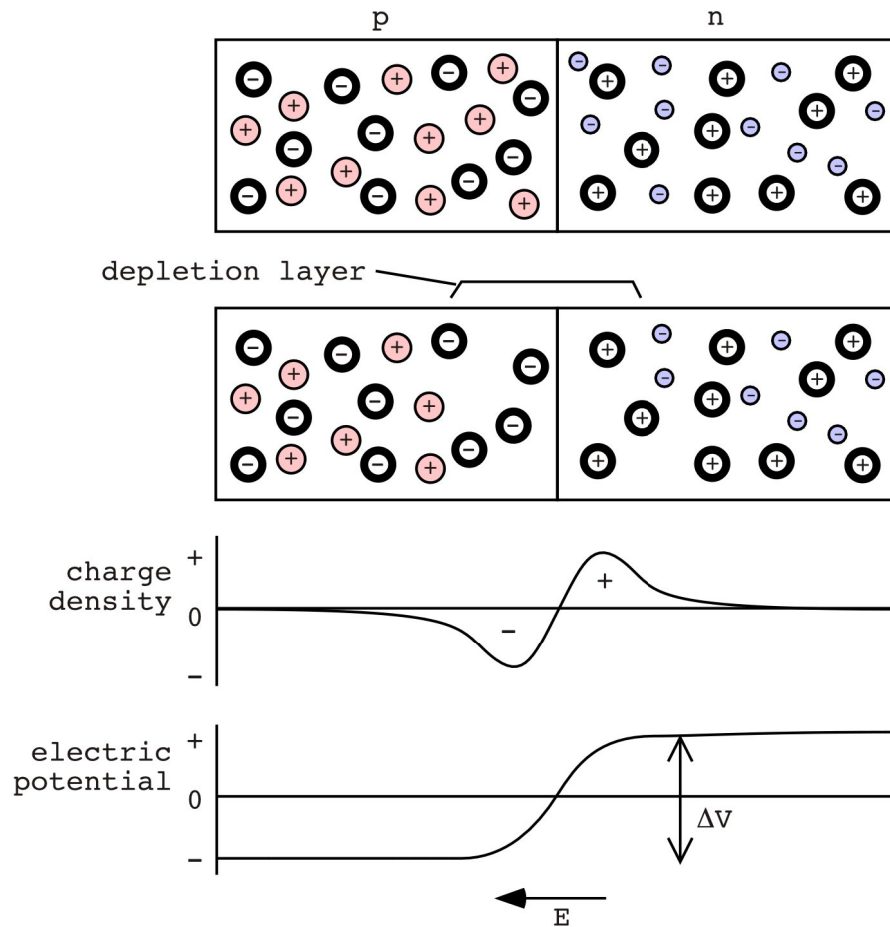$\Delta V \sim 0.6 \text{ V for Si; } \sim 0.3 \text{ V for Ge}$




Forward-biased p-n junction:

- Raise the potential of the p-type side by more than ΔV .
- Holes and electrons flow through the junction.

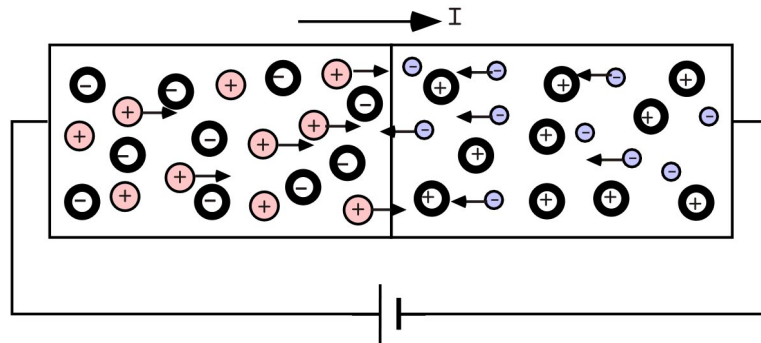
Reverse-biased p-n junction:

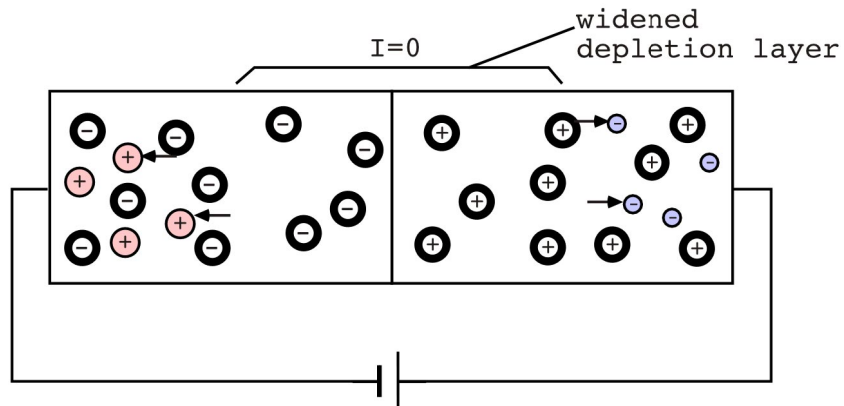- Raise the potential of the n-type side.
- Holes and electrons are pushed away from the junction.
- Depletion layer widens.
- No current flows through the junction.






DIODE

Ideal Diode

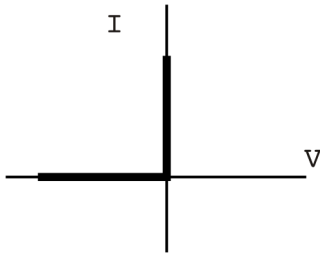

- infinite resistance for reverse bias
- zero resistance for forward bias

p-n Junction Diode

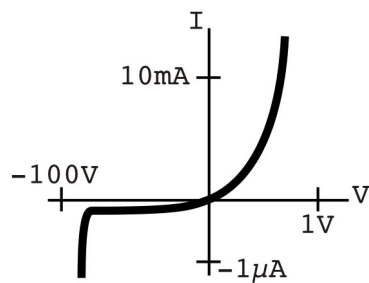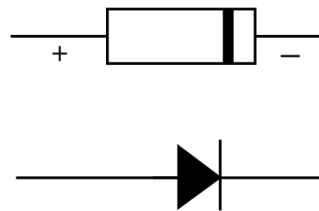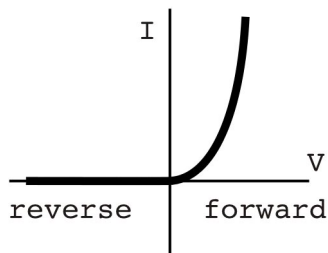

Detail of diode I-V curve:
Note the scales are very different for the forward and reverse directions.

$$I = I_s \left[\exp\left(\frac{eV}{kT}\right) - 1 \right]$$

I_s : reverse saturation current ($\sim 0.1 \mu\text{A}$)

e : electron charge

k : Boltzmann constant

T : temperature


- Diode drop (ΔV_{diode}): $\sim 0.6 \text{ V}$ for silicon; 0.3 V for Ge

Diode Types


- switching diode: low power, high frequency
- rectifier: high current, high power
- LED (light emitting diode): electron-hole recombination > photon emission
forward voltage drop: 1.5~2.5 V; 5~20 mA
- photodiode: electron-hole pair generation by absorption of photon in reverse-biased depletion layer
- Zener diode: non-destructive breakdown at specified reverse voltage; used in voltage regulation
- tunnel diode: high speed switching

DIODE RECTIFIER CIRCUITS


Half-Wave Rectifier

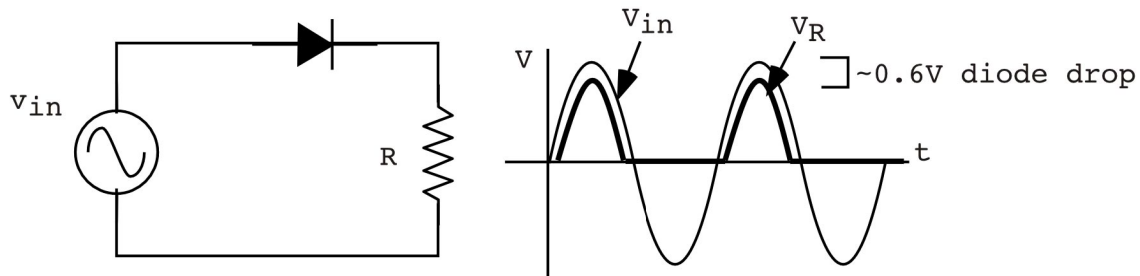

Full-Wave Bridge Rectifier

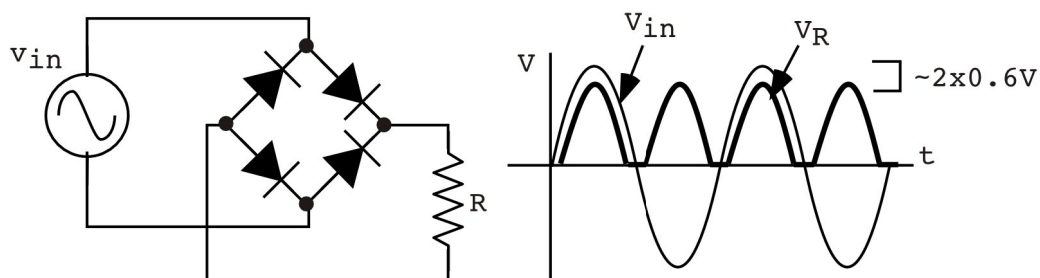

Full-Wave Rectifier with Filtering

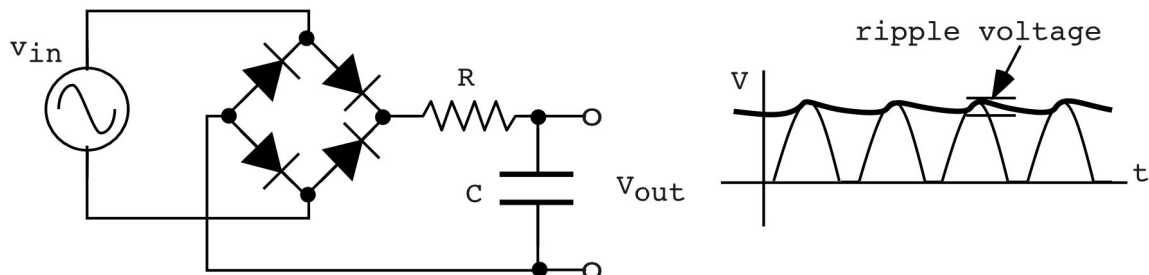

OTHER DIODE CIRCUITS**Diode Clamp**